

# Department of Electronic & Telecommunication Engineering

University of Moratuwa

EN2111 Electronic Circuit Design



## Design UART Implementation in FPGA

Group 38

Name	Index
W. A. D. N. M. Wanniarachchi	210679B
T. R. Wathudura	210682D
M. P. Wickramarathne	210703V

*This is submitted as a partial fulfillment for the module.*

May 8, 2024

## Contents

1. Introduction .....	3
2. Verilog RTL code.....	3
a) Top level module.....	3
b) Transmitter .....	4
c) Receiver .....	5
d) Baudrate.....	6
3. RTL view.....	6
4. Testbench.....	7
5. Simulation results .....	8
6. FPGA implementation .....	8

## 1. Introduction

Universal Asynchronous Receiver Transmitters (UARTs) are widely used communication protocols for serial communication between electronic devices. They are popular due to their simplicity and ease of implementation. In this project, we will implement a UART transceiver system on two separate Field Programmable Gate Arrays (FPGAs) on a DE0-Nano board.

UARTs facilitate asynchronous serial communication, meaning that the data being transmitted does not require a clock signal to synchronize the sender and receiver. This reduces the complexity of the design. UARTs transmit data one bit at a time over a single wire.

Our design will be described using Verilog hardware descriptive language (HDL) and will be simulated using ModelSim software. The DE0-Nano board will be used as the target platform for implementation using Quartus Prime software. This report will detail the design process, including the Verilog code for the UART transmitter and receiver modules, the co-simulation environment setup in ModelSim, and the results of the simulation.

## 2. Verilog RTL Code

### (a) Top level module

```
1 module uart(input wire [7:0] data_in, //input data
2             input wire wr_en,
3             input wire clear,
4             input wire clk_50m,
5             output wire Tx,
6             output wire Tx_busy,
7             input wire Rx,
8             output wire ready,
9             input wire ready_clr,
10            output wire [7:0] data_out,
11            output [7:0] LEDR,
12            output wire Tx2//output data
13        );
14    assign LEDR = data_in;
15    assign Tx2 = Tx;
16    wire Txclk_en, Rxclk_en;
17    baudrate uart_baud( .clk_50m(clk_50m),
18                      .Rxclk_en(Rxclk_en),
19                      .Txclk_en(Txclk_en)
20        );
21    transmitter uart_Tx( .data_in(data_in),
22                      .wr_en(wr_en),
23                      .clk_50m(clk_50m),
24                      .clken(Txclk_en), //We assign Tx clock to enable clock
25                      .Tx(Tx),
26                      .Tx_busy(Tx_busy)
27    );
```

```

28 receiver uart_Rx( .Rx(Rx),
29                 .ready(ready),
30                 .ready_clr(ready_clr),
31                 .clk_50m(clk_50m),
32                 .clken(Rxclk_en), //We assign Tx clock to enable clock
33                 .data(data_out)
34                 );
35
36 endmodule
37

```

## (b) Transmitter

```

1 module transmitter( input wire [7:0] data_in, //input data as an 8-bit register/vector
2                   input wire wr_en, //enable wire to start
3                   input wire clk_50m,
4                   input wire clken, //clock signal for the transmitter
5                   output reg Tx, //a single 1-bit register variable to hold transmitting bit
6                   output wire Tx_busy //transmitter is busy signal
7                   );
8
9 initial begin
10     Tx = 1'b1; //initialize Tx = 1 to begin the transmission
11 end
12 //Define the 4 states using 00,01,10,11 signals
13 parameter TX_STATE_IDLE = 2'b00;
14 parameter TX_STATE_START = 2'b01;
15 parameter TX_STATE_DATA = 2'b10;
16 parameter TX_STATE_STOP = 2'b11;
17
18 reg [7:0] data = 8'h00; //set an 8-bit register/vector as data, initially equal to 00000000
19 reg [2:0] bit_pos = 3'h0; //bit position is a 3-bit register/vector, initially equal to 000
20 reg [1:0] state = TX_STATE_IDLE; //state is a 2 bit register/vector, initially equal to 00
21
22 always @(posedge clk_50m) begin
23     case (state) //Let us consider the 4 states of the transmitter
24     TX_STATE_IDLE: begin //We define the conditions for idle or NOT-BUSY state
25         if (~wr_en) begin
26             state <= TX_STATE_START; //assign the start signal to state
27             data <= data_in; //we assign input data vector to the current data
28             bit_pos <= 3'h0; //we assign the bit position to zero
29         end
30     end
31     TX_STATE_START: begin //We define the conditions for the transmission start state
32         if (clken) begin
33             Tx <= 1'b0; //set Tx = 0 indicating transmission has started
34             state <= TX_STATE_DATA;
35         end
36     end
37     TX_STATE_DATA: begin
38         if (clken) begin
39             if (bit_pos == 3'h7) //we keep assigning Tx with the data until all bits have been transmitted from
40                 state <= TX_STATE_STOP; // when bit position has finally reached 7, assign state to stop transmi:
41             else
42                 bit_pos <= bit_pos + 3'h1; //increment the bit position by 001
43                 Tx <= data[bit_pos]; //Set Tx to the data value of the bit position ranging from 0-7
44             end
45         end
46     end
47     TX_STATE_STOP: begin
48         if (clken) begin
49             Tx <= 1'b1; //set Tx = 1 after transmission has ended
50             state <= TX_STATE_IDLE; //Move to IDLE state once a transmission has been completed
51         end
52     end
53     default: begin
54         Tx <= 1'b1; // always begin with Tx = 1 and state assigned to IDLE
55         state <= TX_STATE_IDLE;
56     end
57 endcase
58 end
59 assign Tx_busy = (state != TX_STATE_IDLE); //We assign the BUSY signal when the transmitter is not idle
60
61 endmodule
62

```

### (c) Receiver

```
1 module receiver (input wire Rx,
2   output reg ready, // default 1 bit reg
3   input wire ready_clr,
4   input wire clk_50m,
5   input wire clken,
6   output reg [7:0] data // 8 bit register
7   );
8 initial begin
9   ready = 1'b0; // initialize ready = 0
10  data = 8'b0; // initialize data as 00000000
11 end
12 // Define the 4 states using 00,01,10 signals
13 parameter RX_STATE_START = 2'b00;
14 parameter RX_STATE_DATA = 2'b01;
15 parameter RX_STATE_STOP = 2'b10;
16
17 reg [1:0] state = RX_STATE_START; // state is a 2-bit register/vector, initially equal to 00
18 reg [3:0] sample = 0; // This is a 4-bit register
19 reg [3:0] bit_pos = 0; // bit position is a 4-bit register/vector, initially equal to 000
20 reg [7:0] scratch = 8'b0; // An 8-bit register assigned to 00000000
21
22 always @(posedge clk_50m) begin
23   if (ready_clr)
24     ready <= 1'b0; // This resets ready to 0
25
26   if (clken) begin
27     case (state) // Let us consider the 3 states of the receiver
28     RX_STATE_START: begin // We define conditions for starting the receiver
29       if (!Rx || sample != 0) // start counting from the first low sample
30         sample <= sample + 4'b1; // increment by 0001
31       if (sample == 15) begin // once a full bit has been sampled
32         state <= RX_STATE_DATA; // start collecting data bits
33         bit_pos <= 0;
34         sample <= 0;
35         scratch <= 0;
36       end
37     end
38     RX_STATE_DATA: begin // We define conditions for starting the data collecting
39       sample <= sample + 4'b1; // increment by 0001
40       if (sample == 4'h8) begin // we keep assigning Rx data until all bits have 01 to 7
41         scratch[bit_pos[2:0]] <= Rx;
42         bit_pos <= bit_pos + 4'b1; // increment by 0001
43       end
44       if (bit_pos == 8 && sample == 15) // when a full bit has been sampled and
45         state <= RX_STATE_STOP; // bit position has finally reached 7, assign state to stop
46     end
47     RX_STATE_STOP: begin
48       /*
49        * Our baud clock may not be running at exactly the
50        * same rate as the transmitter. If we think that
51        * we're at least half way into the stop bit, allow
52        * transition into handling the next start bit.
53        */
54       if (sample == 15 || (sample >= 8 && !Rx)) begin
55         state <= RX_STATE_START;
56         data <= ~scratch;
57         ready <= 1'b1;
58         sample <= 0;
59       end
60       else begin
61         sample <= sample + 4'b1;
62       end
63     end
64     default: begin
65       state <= RX_STATE_START; // always begin with state assigned to START
66     end
67   endcase
68 end
69 end
70
71 endmodule
72
```


### (d) Baudrate

```

4 module baudrate (input wire clk_50m,
5                   output wire Rxclk_en,
6                   output wire Txclk_en
7                   );
8   //Our Testbench uses a 50 MHz clock.
9   //Want to interface to 115200 baud UART for Tx/Rx pair
10  //Hence, 50000000 / 115200 = 435 Clocks Per Bit.
11  parameter RX_ACC_MAX = 50000000 / (115200 * 16);
12  parameter TX_ACC_MAX = 50000000 / 115200;
13  parameter RX_ACC_WIDTH = $clog2(RX_ACC_MAX);
14  parameter TX_ACC_WIDTH = $clog2(TX_ACC_MAX);
15  reg [RX_ACC_WIDTH - 1:0] rx_acc = 0;
16  reg [TX_ACC_WIDTH - 1:0] tx_acc = 0;
17
18  assign Rxclk_en = (rx_acc == 5'd0);
19  assign Txclk_en = (tx_acc == 9'd0);
20
21  always @(posedge clk_50m) begin
22    if (rx_acc == RX_ACC_MAX[RX_ACC_WIDTH - 1:0])
23      rx_acc <= 0;
24    else
25      rx_acc <= rx_acc + 5'b1; //increment by 00001
26  end
27
28  always @(posedge clk_50m) begin
29    if (tx_acc == TX_ACC_MAX[TX_ACC_WIDTH - 1:0])
30      tx_acc <= 0;
31    else
32      tx_acc <= tx_acc + 9'b1; //increment by 000000001
33  end
34
35  endmodule
36

```


### 3. RTL view

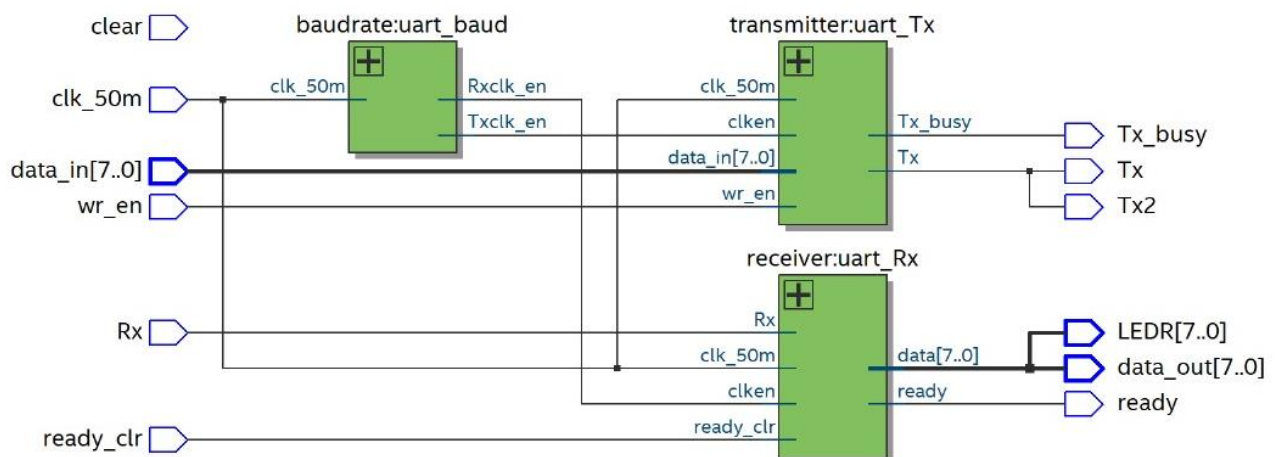

## 4. Testbench

```
1 //This is a simple testbench for UART Tx and Rx.
2 //The Tx and Rx pins have been connected together creating a serial loopback.
3 //We check if we receive what we have transmitted by sending incrementing data bytes.
4
5 //It sends out byte 0xAB over the transmitter
6 //It then exercises the receive by receiving byte 0x3F
7 //`include "uart.v"
8
9 module uart_TB();
10
11 reg [7:0] data = 0;
12 reg clk = 0;
13 reg enable = 0;
14
15 wire Tx_busy;
16 wire rdy;
17 wire [7:0] Rx_data;
18
19 wire loopback;
20 reg ready_clr = 0;
21
22 uart test_uart(.data_in(data),
23                .wr_en(enable),
24                .clk_50m(clk),
25                .Tx(loopback),
26                .Tx_busy(Tx_busy),
27                .Rx(loopback),
28                .ready(ready),
29                .ready_clr(ready_clr),
30                .data_out(Rx_data)
31                );
32
33 initial begin
34     $dumpfile("uart.vcd");
35     $dumpvars(0, uart_TB);
36     enable <= 1'b1;
37     #2 enable <= 1'b0;
38 end
39
40 always begin
41     #1 clk = ~clk;
42 end
43
44 always @(posedge ready) begin
45     #2 ready_clr <= 1;
46     #2 ready_clr <= 0;
47     if (Rx_data != data) begin
48         $display("FAIL: rx data %x does not match tx %x", Rx_data, data);
49         $finish;
50     end
51     else begin
52         if (Rx_data == 8'h2) begin //Check if received data is 11111111
53             $display("SUCCESS: all bytes verified");
54             $finish;
55         end
56         data <= data + 1'b1;
57         enable <= 1'b1;
58         #2 enable <= 1'b0;
59     end
60 end
61 endmodule
```

## 5. Simulation Results

 

## 6. FPGA implementation

